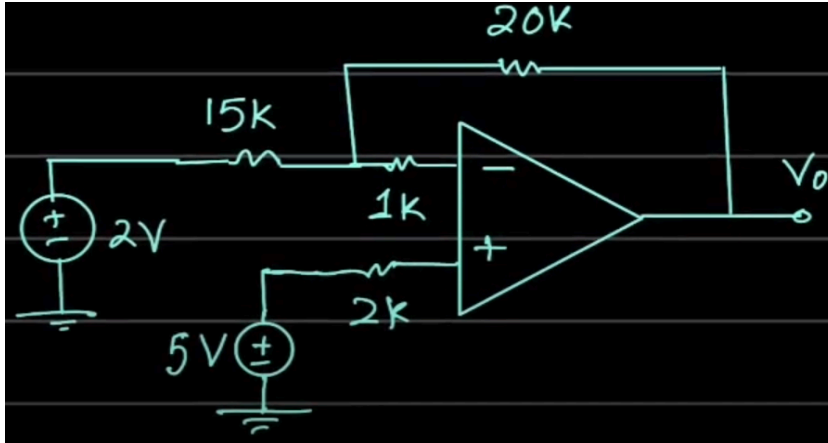


17. Miscellaneous

Determine the output voltage, v_o




Solution: (from central playlist)

<https://youtu.be/KBWfa-NuYzk?list=PLPf6M92pkd7DRilBZLzKot-39S215ksSw&t=617>

18. Miscellaneous

Determine the output voltage, v_o

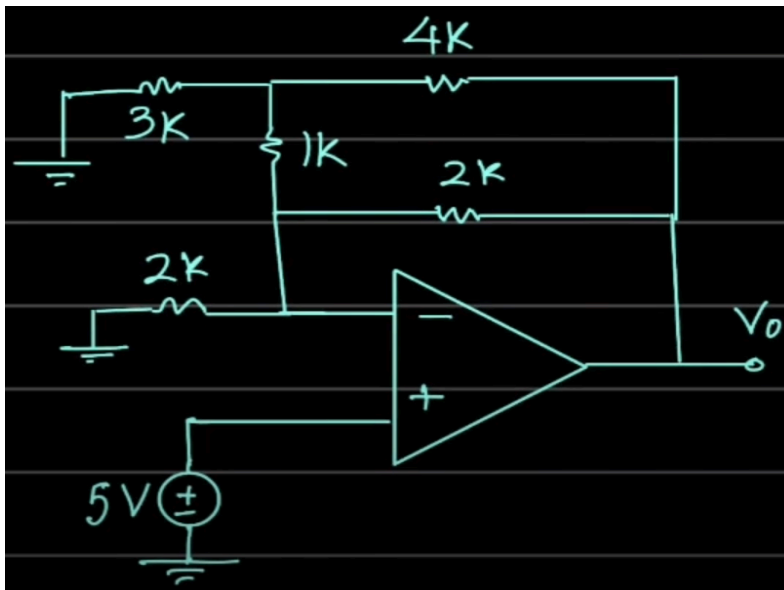


Solution: (from central playlist)

<https://youtu.be/KBWfa-NuYzk?list=PLPf6M92pkd7DRilBZLzKot-39S215ksSw&t=890>

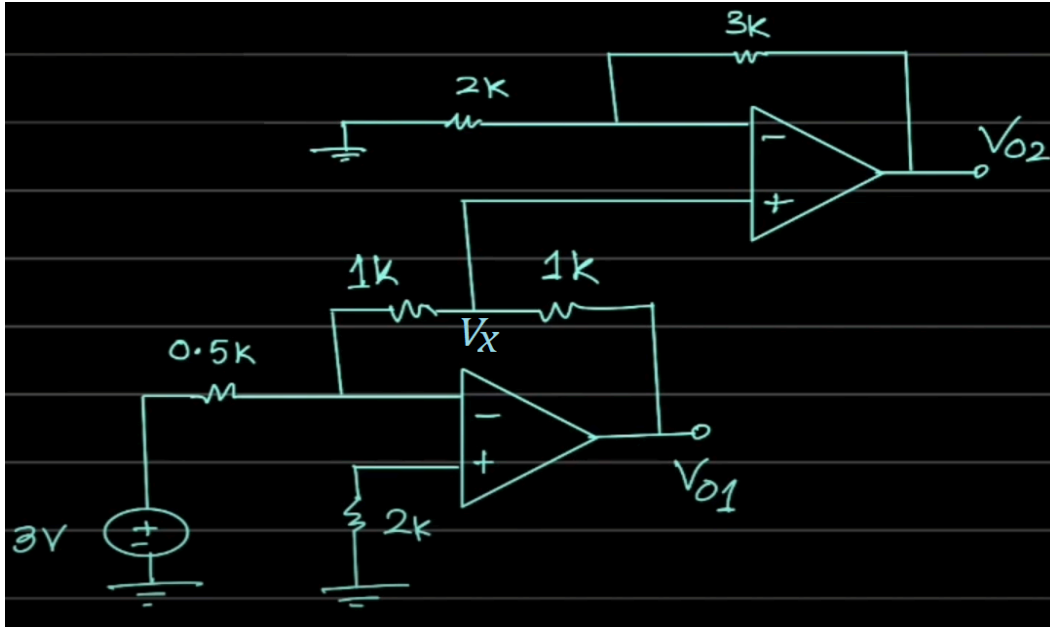19. Miscellaneous

Determine the voltages: V_{o1} , V_x , V_{o2}




Solution: (from central playlist)


<https://youtu.be/KBWfa-NuYzk?list=PLPf6M92pkd7DRilBZLzKot-39S215ksSw&t=1198>

Additional Hint for finding V_x : Use Nodal Analysis on the V_x node instead of the current method shown in the video link above.

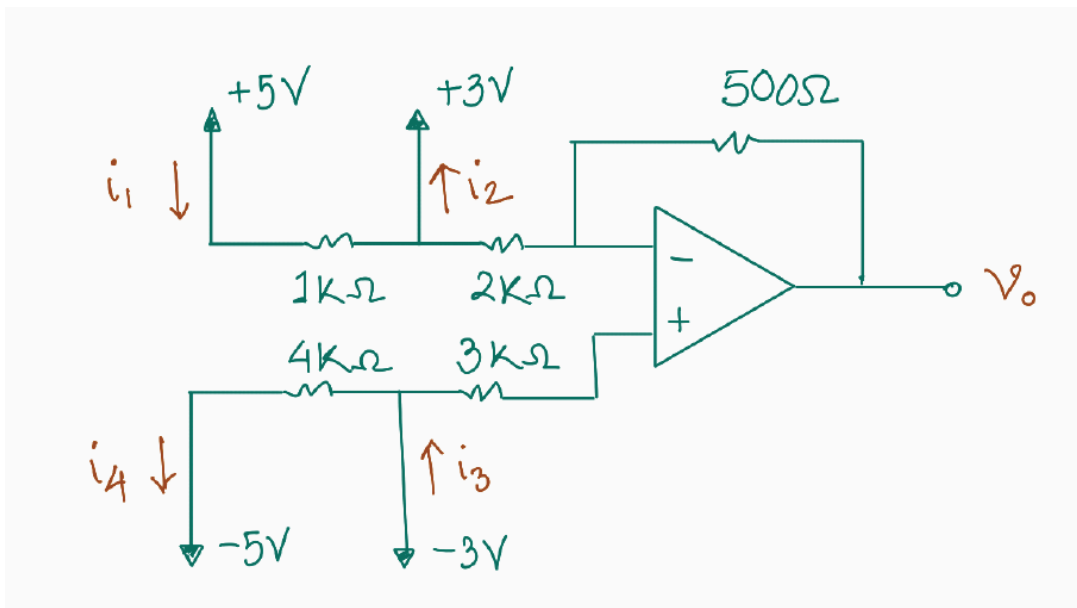20. Miscellaneous


Determine the marked currents and the output voltage



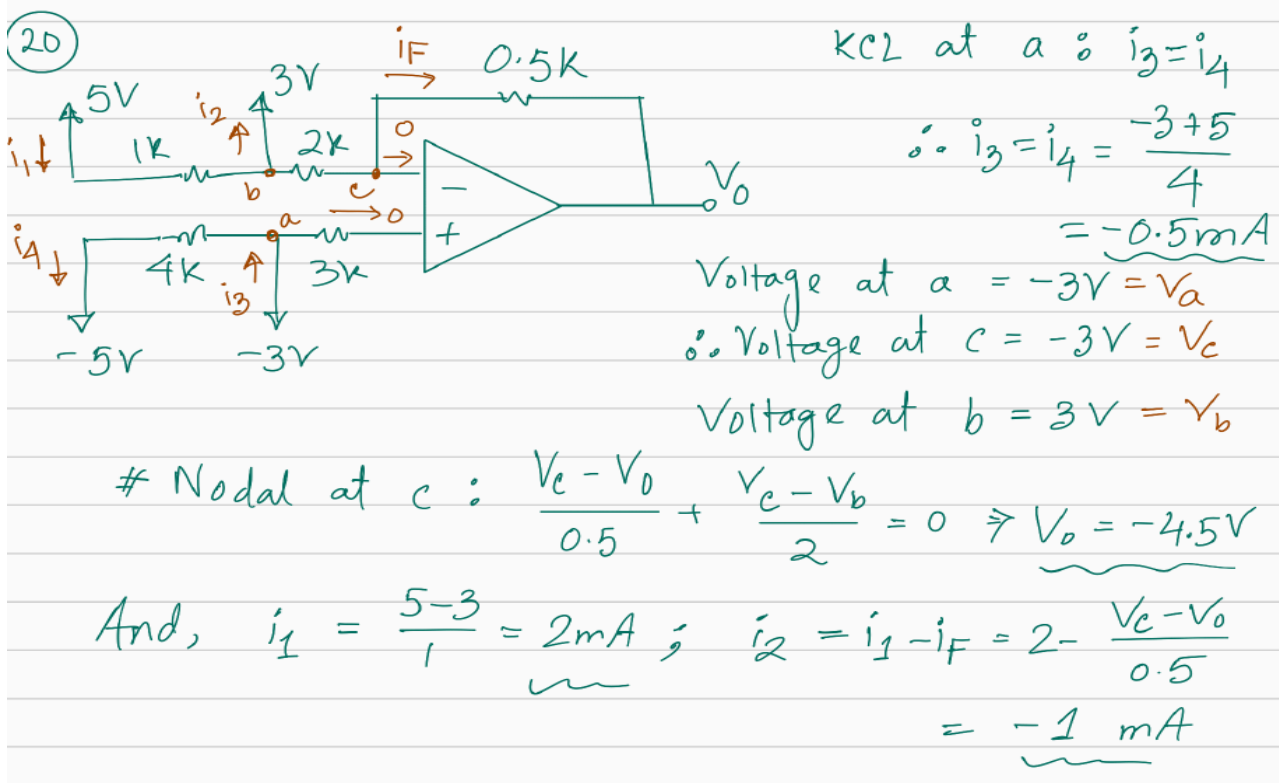


21. Miscellaneous

Determine the appropriate value of R_1

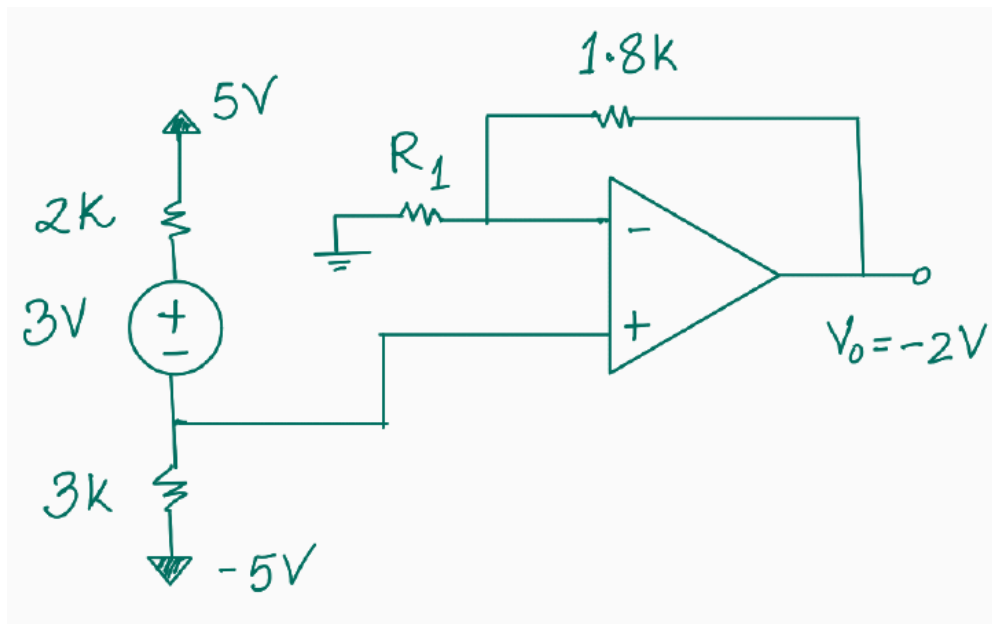

(21)

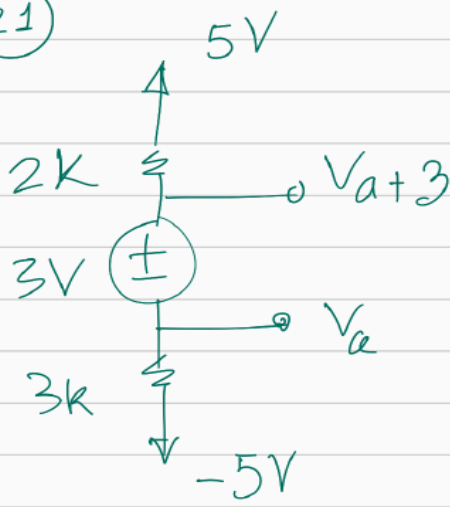

Nodal at V_a & (V_a+3) :

$$\frac{V_a+5}{3} + \frac{V_a+3-5}{2} = 0$$

$$\Rightarrow V_a = -0.8V$$


V_a is connected to a non-inverting amplifier

$$\therefore V_o = -2 = V_a \left(1 + \frac{1.8}{R_1}\right)$$

Solve for R_1

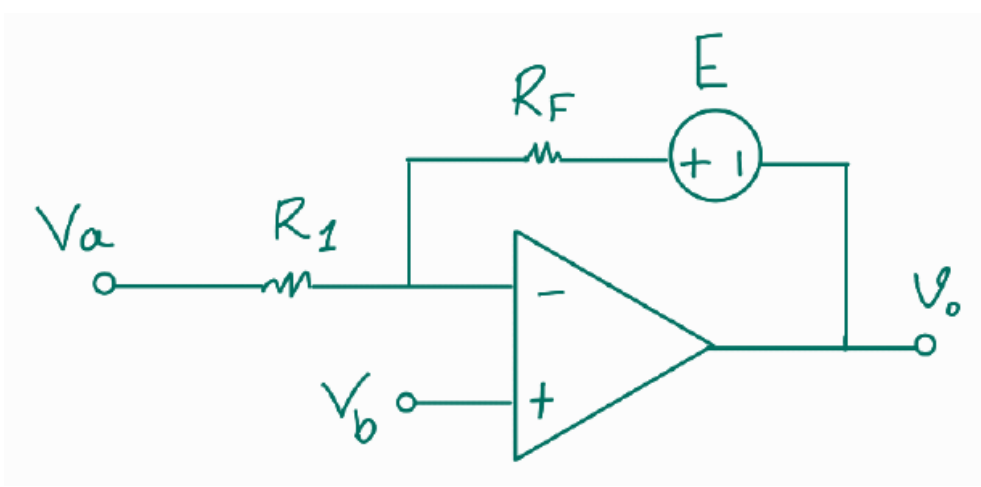
22. Miscellaneous

Express the output voltage v_o in terms of all the other quantities shown in the circuit below.



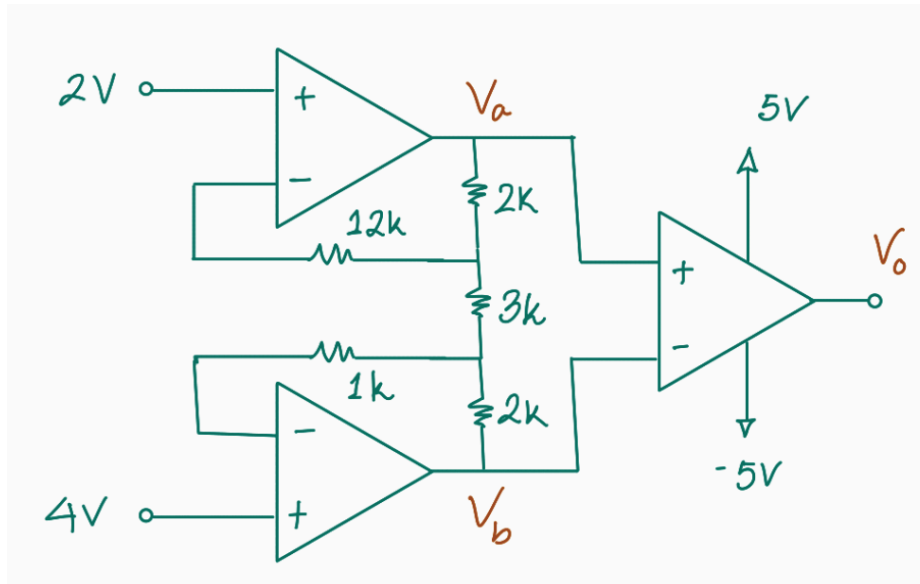23. Miscellaneous

Determine the output of the comparator, V_o after finding V_a and V_b .



23

Applying Nodal on the x :

$$\frac{x - V_a}{2} + \frac{x - y}{3} = 0$$


$$\Rightarrow \frac{2 - V_a}{2} + \frac{2 - 4}{3} = 0 \Rightarrow V_a = 0.67V$$

Also Nodal on y node : $V_b = 5.33V$

* For the comparator : $V_a < V_b$
 $\Rightarrow V^+ < V^-$
 $\therefore V_o = -5V$

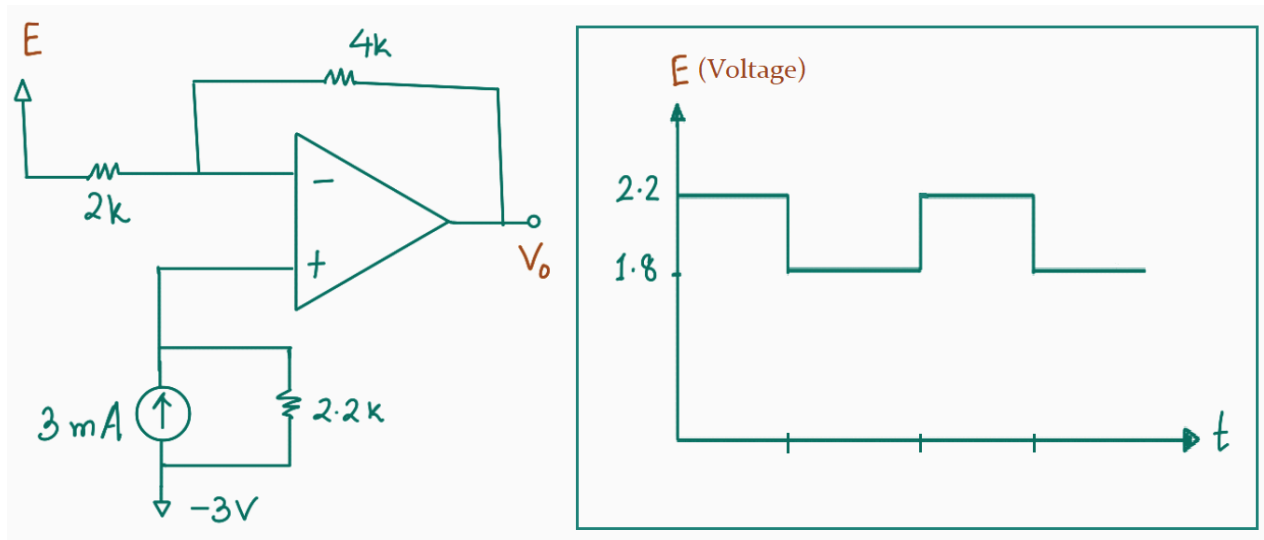24. Miscellaneous

Draw the correct waveform of V_0 (with voltage labels) alongside the input waveform of E .



$$V^+ = -3 + (2.2 * 3) = 3.6\text{ V [you may use source transformation here too]}$$


$$V^+ = V^- = 3.6\text{ V}$$

When $E = 2.2\text{ V} \Rightarrow$ Nodal Analysis at V^- :

$$(V^- - 2.2)/2 + (V^- - V_0)/4 = 0 \Rightarrow V_0 = 6.4\text{ V}$$

When $E = 1.8\text{ V} \Rightarrow$ Nodal Analysis at V^- :
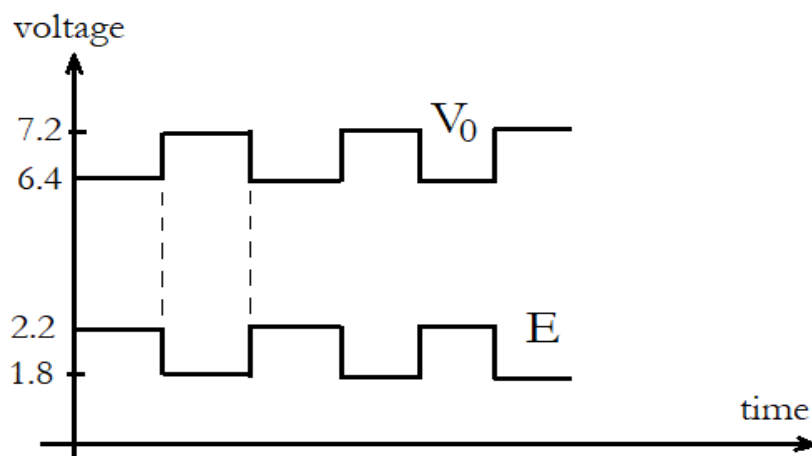
$$(V^- - 1.8)/2 + (V^- - V_0)/4 = 0 \Rightarrow V_0 = 7.2\text{ V}$$



25. Miscellaneous



We know that the input-output relationship of an ideal inverting amplifier with op-amp is given by:

$$V_o = -\frac{R_F}{R_1} V_{in}$$

However, realistic op-amps are non-ideal. Determine the input-output relationship of a **non-ideal inverting amplifier**. Use the equivalent circuit of an op-amp which contains A , R_i , R_o .

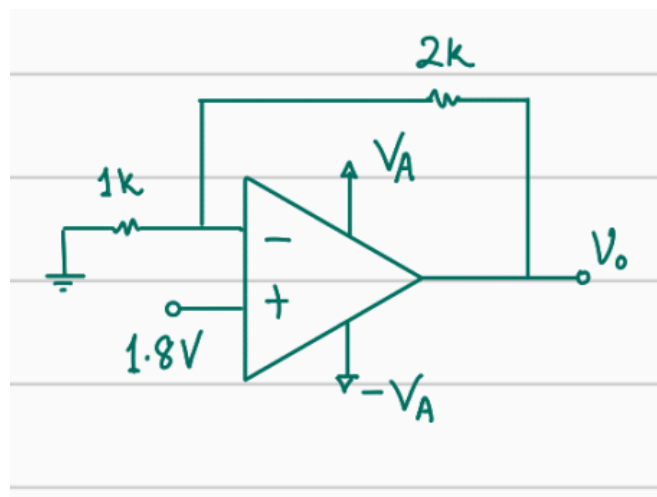
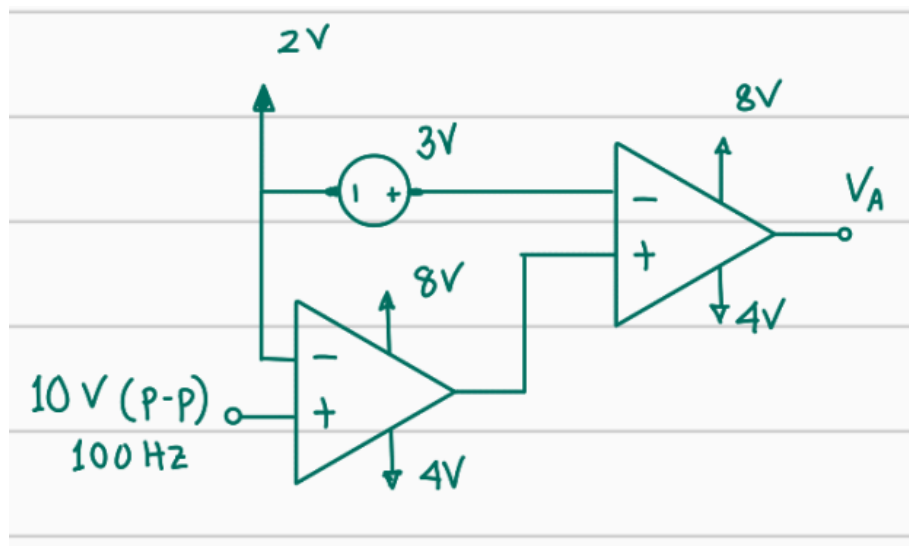
26. Miscellaneous

Draw the approximate waveforms of both V_A and v_o from the circuit below.



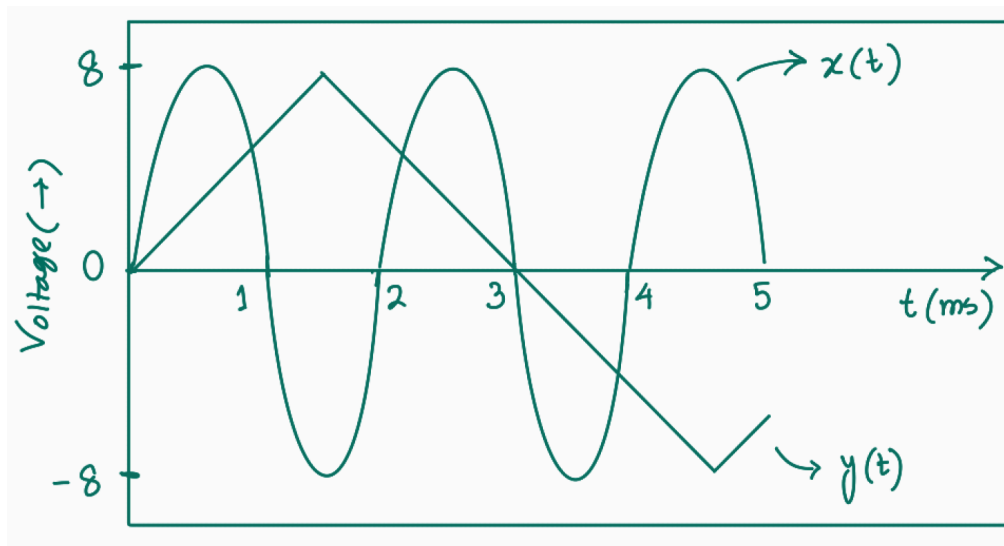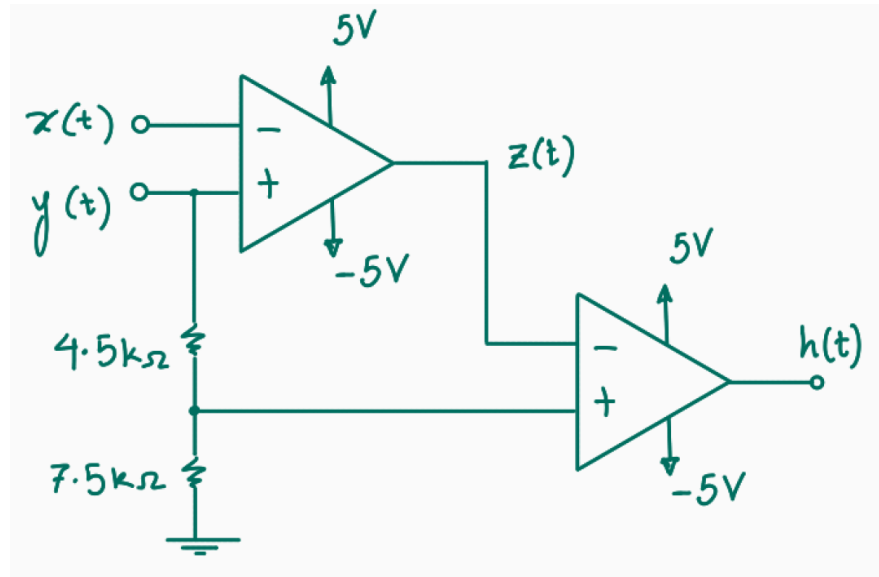27. Miscellaneous

After drawing both $z(t)$ and $h(t)$, determine the relation between them.




28. Miscellaneous

Draw the VTC of both an inverting and a non-inverting amplifier. The following information are known:

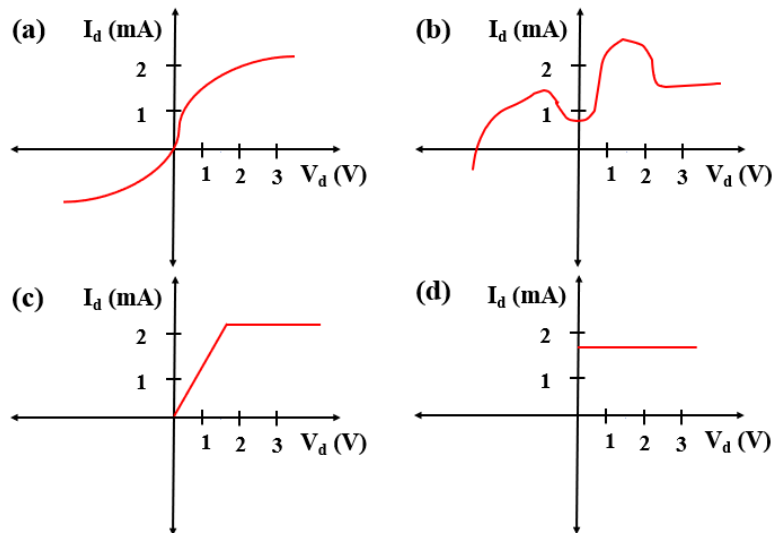(i) $2R_1 = R_F$ (ii) $V_{sat}^+ = +10\text{V}$, $V_{sat}^- = -10\text{V}$


I-V

- Identify which of these I-V curves are Linear and which are Nonlinear:




Ans: Linear: (d)

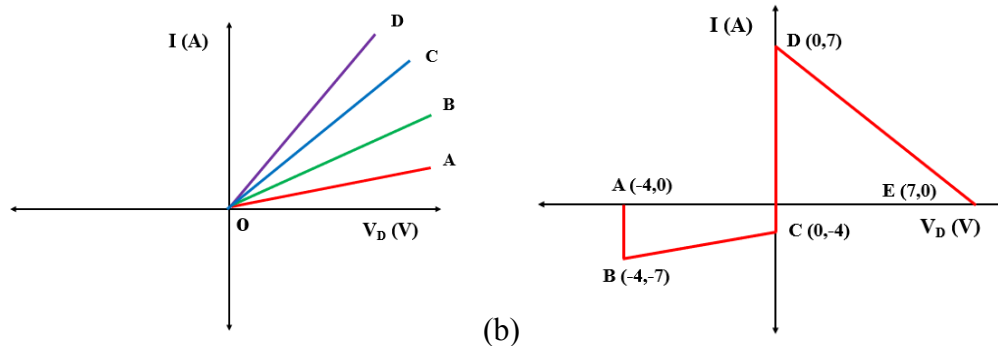- Write down the slopes of these following regions in ascending order (you do not need to calculate the slopes)



Ans: (a) $|OA| < |OB| < |OC| < |OD|$, (b) Slopes of AB and CD are equal(infinity). The DE slope is negative. However, the value of slope is higher than BC here. $|BC| < |DE| < |AB|$

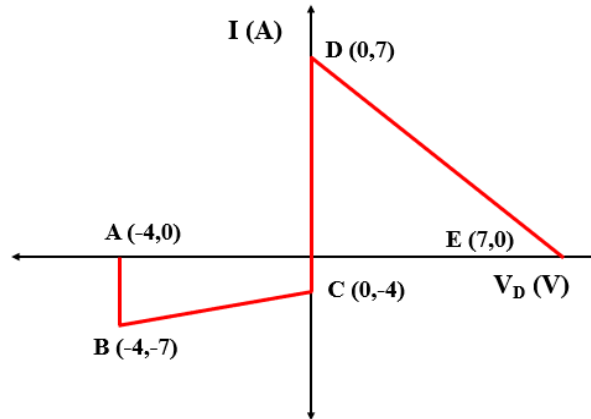- Find out the slope of the following curves



Answer: **Slope, $|m| = \left| \frac{y_2 - y_1}{x_2 - x_1} \right|$**

$$|BC| = \left| \frac{y_2 - y_1}{x_2 - x_1} \right| = \left| \frac{-7 - 4}{-4 - 0} \right| = \frac{3}{4}$$

$$|DE| = \left| \frac{y_2 - y_1}{x_2 - x_1} \right| = \left| \frac{0 - 7}{7 - 0} \right| = 1 \text{ [Can you identify the issue in this curve?]}$$

$$|AB| = \left| \frac{y_2 - y_1}{x_2 - x_1} \right| = \left| \frac{-7 - 0}{-4 - 4} \right| = \infty$$

- Calculate and Show 'C' and 'Io' in the figures

[Hint: use $-\frac{V_o}{R} = I_o = c$]

- Draw the alternative circuit diagram, I-V curve and calculate the parameters with the following information:

i. $V_o = 5V$, $m = 2/k\Omega$

ii. $V_o = 3.5V$, $m = -2.5/k\Omega$

iii. $V_o = -5V$, $m = 5/k\Omega$


Solution:

i. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{2} k\Omega$, $c = -\frac{V_o}{R} = -\frac{5}{0.5} mA = -2.5 mA$



ii. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{2.5} k\Omega$, $c = -\frac{3.5}{0.4} mA = -8.75 mA$

iii. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{5} k\Omega$, $c = -\frac{-5}{0.2} mA = 25 mA$

Alternative Diagram:


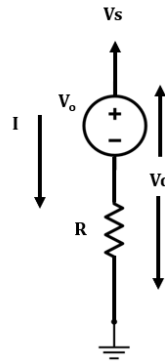


I-V curve:

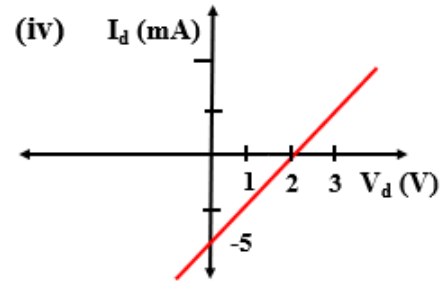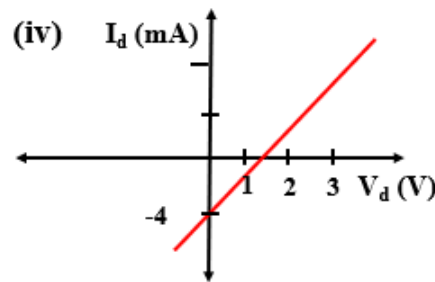

- Calculate and Show 'C' and 'Vo' in the figures

[Hint: Use $I_o R = -V_o$]

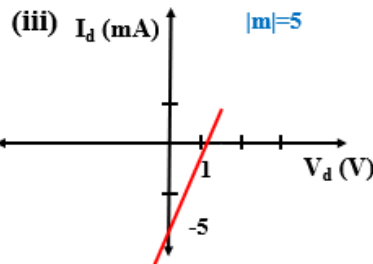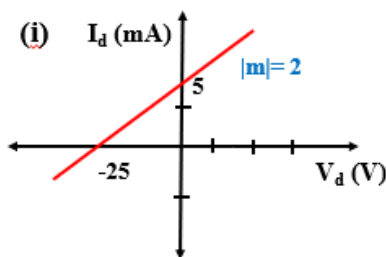

- Draw the alternative circuit diagram with the equivalent linear model, I-V curve and calculate the parameters with the following information:

- $I_o = 5 \text{ mA}$, $m = 2/k\Omega$
- $I_o = 3.5 \text{ mA}$, $m = -2.5/k\Omega$
- $I_o = -5 \text{ mA}$, $m = 5/k\Omega$



Solution:

i. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{2} k\Omega$, $c = I_o = 5 \text{ mA}$, $V_o = -I_o R = -2.5 \text{ V}$

ii. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{2.5} k\Omega$, $c = I_o = 3.5 \text{ mA}$, $V_o = -(-I_o R) = 1.4 \text{ V}$; as m is negative


iii. $|R| = \left| \frac{1}{m} \right|$ i.e. $\frac{1}{5} k\Omega$, $c = I_o = -5 \text{ mA}$, $V_o = -I_o R = 1 \text{ V}$

Alternative diagram:

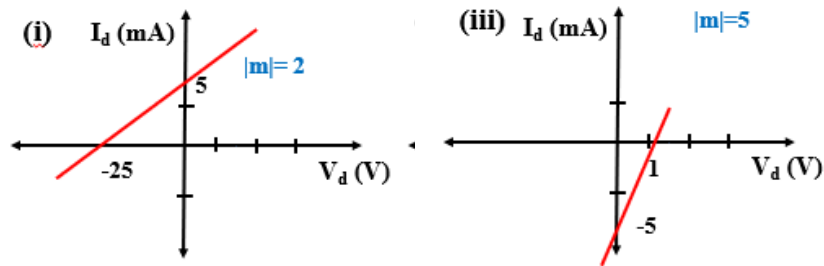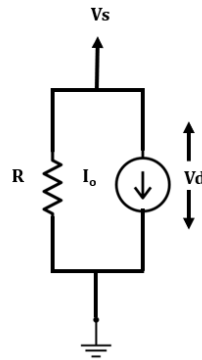

I-V:

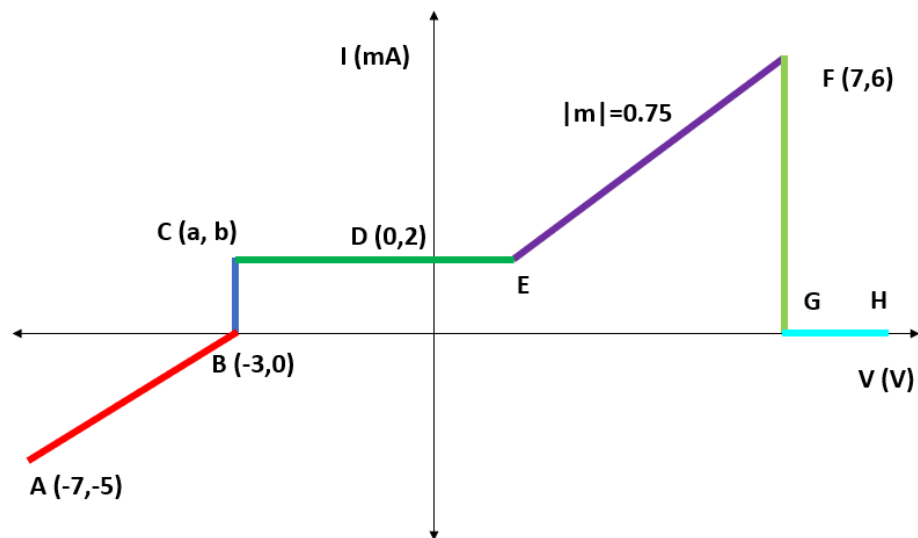- From the I-V curve-
 - State the device model for each region,



Solution:

i.

AB: Voltage source in series with a resistor/ Current source in parallel with a resistor

BC: Voltage source

CD: Current source

EF: Voltage source in series with a resistor/ Current source in parallel with a resistor

FG: Voltage source

- A Voltage Source, $V_o = 10\text{ V}$ in series with a resistor of $R = 3\text{ k}\Omega$.
 - i. Write down the equation representing this curve
 - ii. Determine the unknown parameters
 - iii. Label the I-V curve

Solution:

i. $y = mx + c$

Or, $I = m \cdot V_s - \frac{V_o}{R}$


ii. $V_o = 10\text{ V}$, $R = 3\text{ k}\Omega$

$$|m| = \left| \frac{1}{R} \right| = \frac{1}{3}$$

Y axis intersection: $c = -\frac{V_o}{R} = -\frac{10\text{V}}{3\text{k}\Omega} = -\frac{10}{3}\text{ mA}$

X axis intersection: $V_o = 10\text{ V}$

iii.

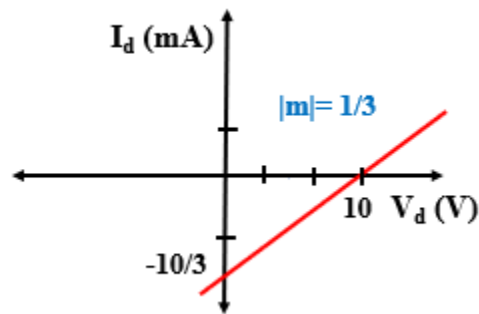

- A Voltage Source, $V_o = -10\text{ V}$ in series with a resistor of $R = 3\text{ k}\Omega$.
 - i. Write down the equation representing this curve
 - ii. Determine the unknown parameters
 - iii. Label the I-V curve

Solution:

i. $y = mx + c$

Or, $I = m \cdot V_s - \frac{V_o}{R}$


ii. $V_o = 10\text{ V}$, $R = 3\text{ k}\Omega$

$$|m| = \left| \frac{1}{R} \right| = \frac{1}{3}$$

Y axis intersection: $c = -\frac{V_o}{R} = -\frac{-10\text{V}}{3\text{k}\Omega} = \frac{10}{3}\text{ mA}$

X axis intersection: $V_o = -10\text{ V}$

Iii.

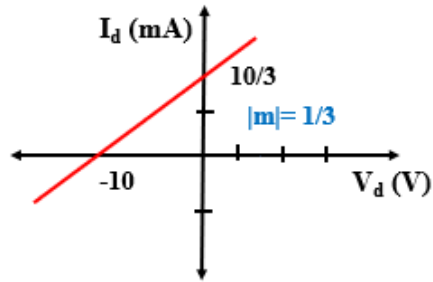

- A Current Source, $I_o = 5 \text{ mA}$ in parallel with a resistor of $R = 5 \text{ k}\Omega$.

- Write down the equation representing this curve
- Determine the unknown parameters
- Label the I-V curve

Solution:

i. $y = mx + c$

Or, $I_s = \frac{V_s}{R} + I_o$

ii. $V_o = 10 \text{ V}$, $R = 5 \text{ k}\Omega$


$|m| = \left| \frac{1}{R} \right| = \frac{1}{5}$

Y axis intersection : $c = I_o = 5 \text{ mA}$

X axis intersection: $I_o R = -V_o$

Or, $V_o = -5 \times 5 \text{ V} = -25 \text{ V}$



iii.

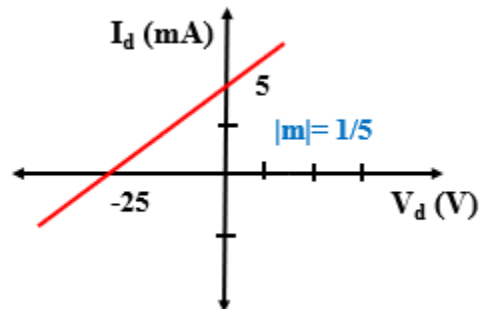

- You are provided with the following circuit elements:


- Two $1\text{ k}\Omega$ resistors
- A 4 V voltage source
- A 2 V voltage source

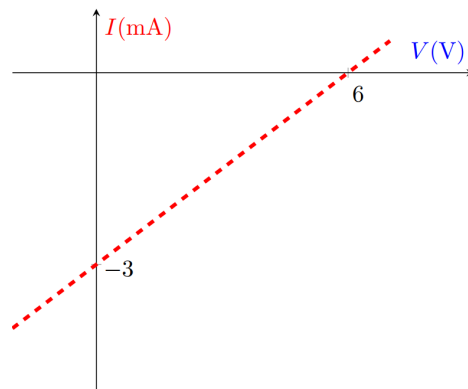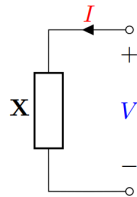Can you implement a circuit element X that has an IV characteristics, as seen in the right figure below, but by **ONLY USING THE ELEMENTS MENTIONED ABOVE**? The voltage polarity and current direction should be as shown in the left figure.



Hybrid Problems


1.

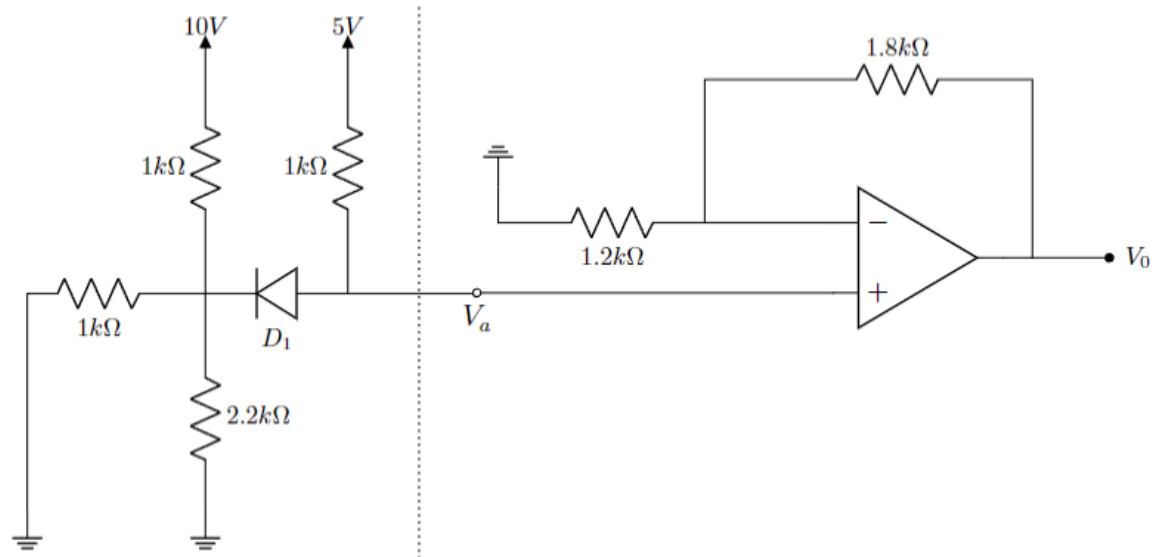

The saturation voltages of the Op-Amp are given as- $V_{sat}^+ = +10V$ and $V_{sat}^- = -10V$. The forward voltage drop of the diode, V_D is $0.7V$.

- Determine** the operating mode diode, D_1 . Verify your assumption with necessary calculations.
- Calculate** the voltage at - (i) node 'Va', (ii) non-inverting terminal of the Op-Amp, (iii) inverting terminal of the Op-Amp.
- Find out the output voltage, V_o of the Op-Amp.

① Assuming D_1 to be ON:

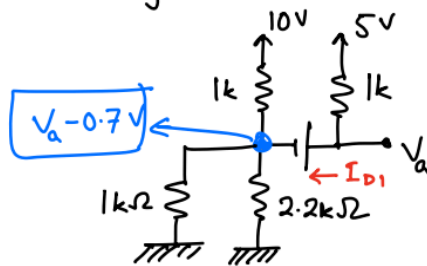

Node equation at supernode (V_a)

$$(V_a - 0.7) \left(1 + 1 + \frac{1}{2.2} \right) + V_a - 10 - 5 = 0$$

$$V_a = 4.84V$$

$$V_a = 4.84V$$

$$I_{D1} =$$


$$= 0.16 \text{ mA} > 0$$

\therefore Assumption true.

(no current flows into op-amp terminals)

$$V_o = (1 + 1.8/1.2) * V_a$$

2.

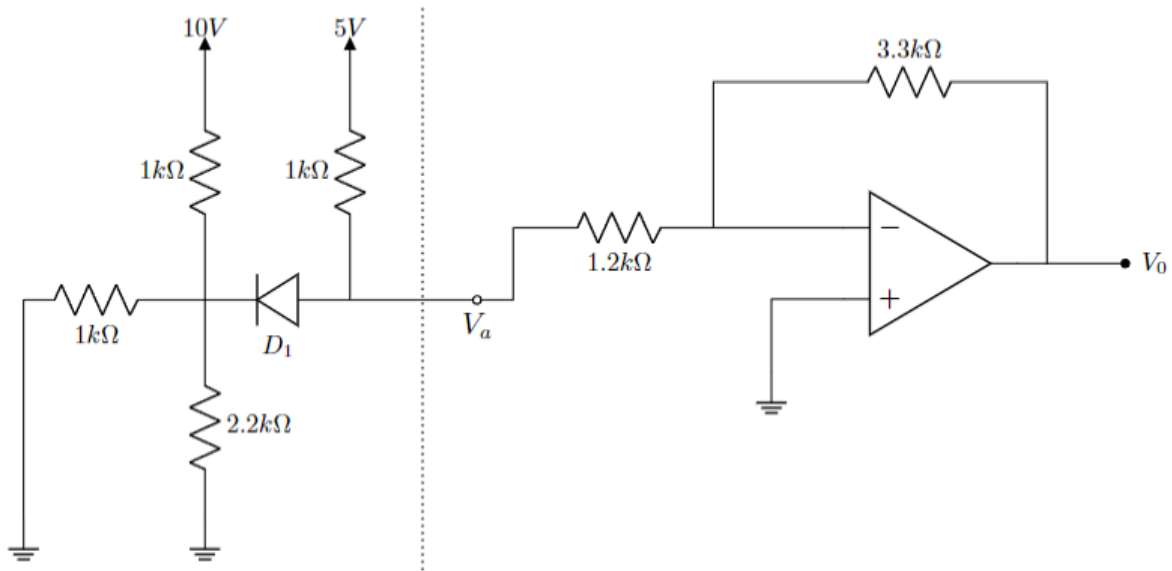


The saturation voltages of the Op-Amp are given as- $V_{sat}^+ = +10V$ and $V_{sat}^- = -10V$. The forward voltage drop of the diode, V_D is $0.7V$.

- Determine** the operating mode diode, D_1 . Verify your assumption with necessary calculations.
- Calculate** the voltage at - (i) node 'Va', (ii) non-inverting terminal of the Op-Amp, (iii) inverting terminal of the Op-Amp.
- Find out the output voltage, V_o of the Op-Amp.

Soln:

Assume D_1 on

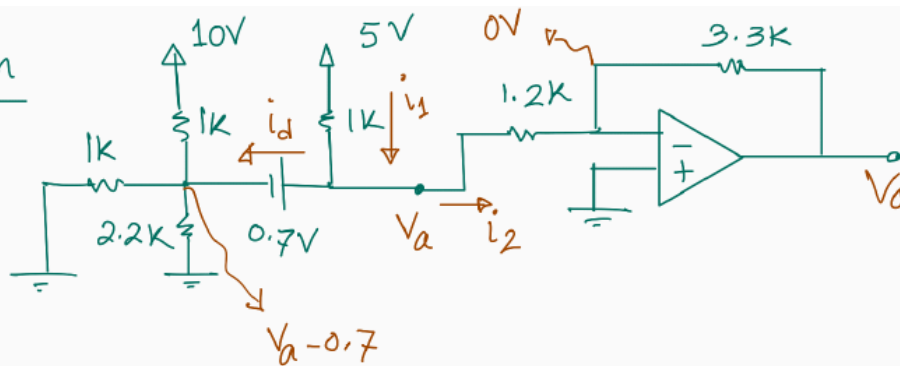


Nodal : $(V_a - 0.7)(1 + 2.2^{-1}) + V_a(1 + 1.2^{-1}) = 10 + 5$

$$\Rightarrow V_a = 3.898 \text{ V}$$

$$\therefore i_d = i_1 - i_2 = \frac{5 - V_a}{1} - \frac{V_a - 0}{1.2} = -2.15 \text{ mA} < 0 \text{ mA}$$

$\therefore D_1$ "cannot" be ON

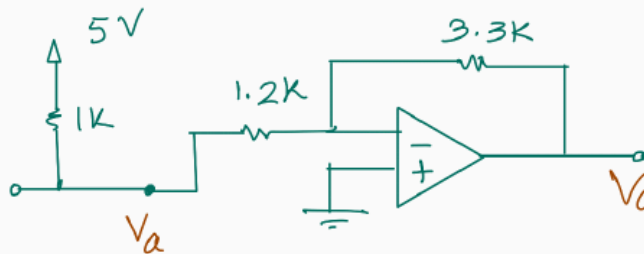$\therefore D_1$ is OFF \rightarrow Left side Open \rightarrow Equivalent ckt :




\Rightarrow This is an inverting amplifier with 5V and $(1\text{k} + 1.2\text{k})$ at the inverting terminal

$$\therefore V_o = - \frac{3.3}{1 + 1.2} \times 5\text{V} = -6.82 \text{ V}$$

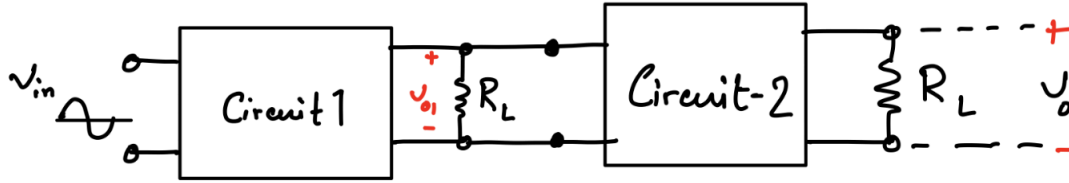3.


You are provided with the diagram below as a starting point for designing an AC to DC converter. Input voltage source is an sinusoidal voltage source (V_{in}), with 2V peak to peak voltage (i.e. 1 V amplitude) and the DC voltage is around 10 V (with ripple) at the output terminals (v_o).



So, in order to solve this problem, you are provided with a single diode (with $V_{D0} = 0.7 \text{ V}$), two resistors (R_1 and R_2 , excluding the load resistors R_L) and an UA741 op-amp.

- Design **circuit-1** with the single diode and $R_L = 10 \text{ k}\Omega$ (R_L is already provided in the diagram as output terminals of **circuit-1**) to get a rectified voltage and determine the DC value of the output voltage (v_{o1}) of the circuit. [1+2]
- Determine the ripple voltage of v_{o1} . [Ripple voltage is defined as the difference between the maximum and minimum value of a DC voltage.] [2]
- What should be the value of a capacitor used at the output end of **circuit-1** with R_L to reduce the ripple voltage of v_{o1} to 0.1 V. How should the capacitor be connected with R_L in the diagram? [4+1]
- Design an amplifier using an operational amplifier as **circuit-2** to increase the DC voltage level of the output voltage of the circuit designed in (c) to 10 V. Find the ripple voltage of the amplified voltage signal. [4+1]

4.

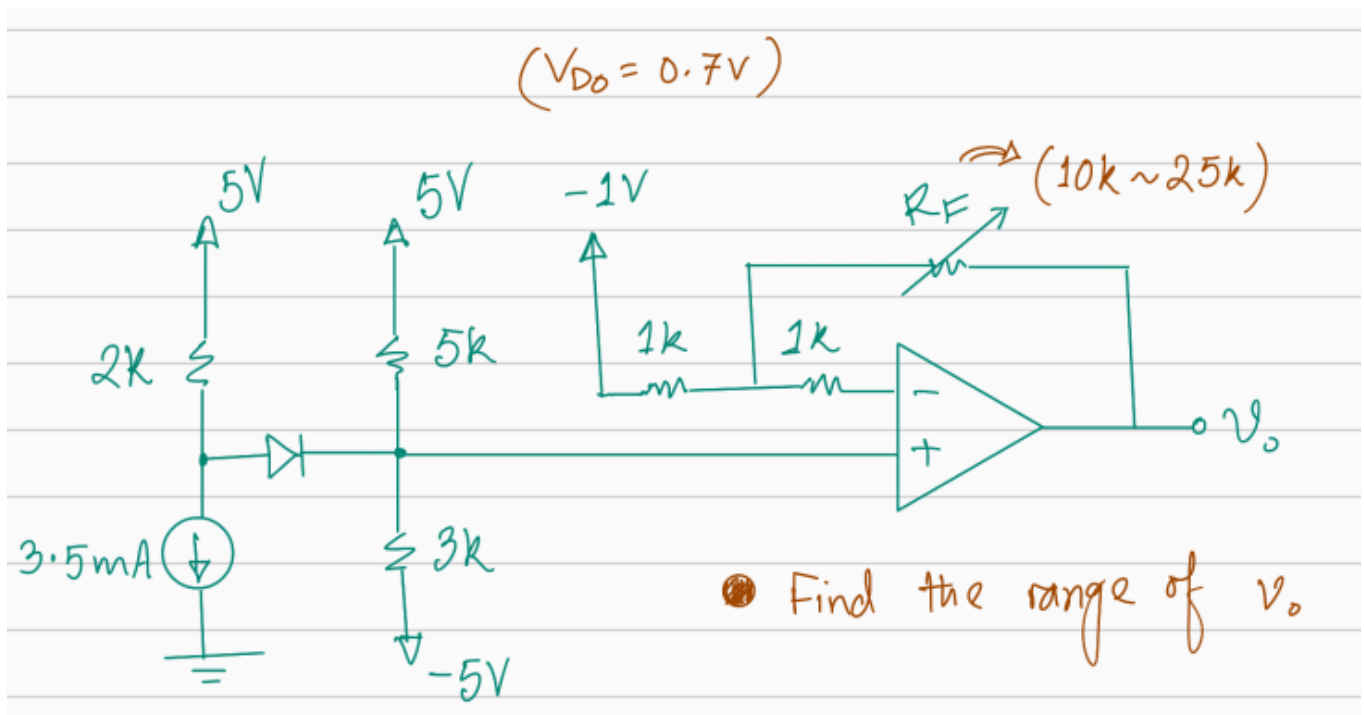

5.

